



# MERU UNIVERSITY OF SCIENCE AND TECHNOLOGY

P.O. Box 972-60200 – Meru-Kenya.  
Tel: +254(0) 799 529 958, +254(0) 799 529 959, +254 (0)712 524 293  
Website: [www.must.ac.ke](http://www.must.ac.ke) Email: [info@mucst.ac.ke](mailto:info@mucst.ac.ke)

## UNIVERSITY EXAMINATIONS 2023/2024

THIRD YEAR, SECOND SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR OF SCIENCE IN (PHYSICS), BACHELOR OF SCIENCE IN PHYSICS AND BACHELOR OF EDUCATION SCIENCE

### SPH 3353: ELECTRONICS II

DATE: APRIL 2024

TIME: 2 HOURS

INSTRUCTIONS: Answer Question ONE and any other TWO questions.

#### QUESTION ONE (30 MARKS)

- a) i. Differentiate between AND and OR gates using truth tables. (2 Marks)  
ii. Convert the decimal number 27 to binary and octal. (2 Marks)  
iii. Perform the following binary addition:  $1011+0101=?$  (2 Marks)  
iv. Convert the hexadecimal number A5 to binary and decimal. (2 Marks)  
v. Briefly explain the purpose of Karnaugh maps in logic minimization. (2 Marks)
- b) i. Explain the function of a 555 timer and give one example of its use. (2 Marks)  
ii. What is the difference between an ADC and a DAC? (2 Marks)  
iii. Briefly explain how DRAM and SRAM memories work. (2 Marks)  
iv. What are the advantages and disadvantages of using flip-flops in digital circuits? (2 Marks)  
v. Describe the basic operation of a ring counter. (2 Marks)
- c) i. Design a simple combinational circuit using only NAND gates to implement the exclusive-OR (XOR) function. (3 Marks)



- ii. Explain the concept of metastability in flip-flops and how it can be mitigated.
- iii. Briefly describe the main differences between CMOS and bipolar transistor logic families. (2 Marks)
- iv. What are the key features and applications of Field-Programmable Gate Arrays (FPGAs)? (2 Marks)

**QUESTION TWO (20 MARKS)**

- a) Define the following terms
  - i. Analog signal (2 Marks)
  - ii. Digital signal (2 Marks)
- b) Briefly explain two key differences between analog and digital signals. (1Mark)
- c) Using a truth table, describe the operation of the following logic gates:
  - i. OR gate
  - ii. AND gate
  - iii. NOT gate
- d) Draw the logic symbol for each of the gates mentioned above (2 Marks)
- e) Design a simple logic circuit using only AND, OR, and NOT gates that outputs a 1 only when both inputs A and B are 0 Draw the circuit diagram and explain its operation. (4 Marks)
- f) Simplify the following Boolean expression using De Morgan's Law. (4 Marks)
- g) Express the following logic function using basic Boolean operators (AND, OR, NOT) Output = 1 only when A and B are different (XOR operation) (4 Marks)

**QUESTION THREE (20 MARKS)**

- a) i. Define a multiplexer and describe its basic operation (2 Marks)
- b) ii. Briefly explain how a 4:1 multiplexer can be used to implement any two-input logic function. Draw a logic diagram demonstrating this concept for the XOR function. (3 Marks)



- c) iii. Design a combinational logic circuit using only a 4:1 multiplexer and additional logic gates (e.g., AND, OR, NOT) to convert a 4-bit Gray code to a 4-bit binary code. Draw the circuit diagram and explain its operation. (3 Marks)
- b) i. Briefly describe the main functions performed by an Arithmetic Logic Unit (ALU) (2 Marks)
- ii. Provide an example of how a 4-bit ALU can be used to perform addition of two 4-bit binary numbers (2 Marks)
- iii. Provide an example of how a 4-bit ALU can be used to perform subtraction of two 4-bit binary numbers (2 Marks)
- c) i. Define the purpose of a digital comparator and explain its basic operation (2 Marks)
- ii. Give an example of how a 4-bit comparator can be used to determine if two 4-bit binary numbers are equal (2 Marks)
- iii. Briefly describe the function of a decoder/driver in the context of displaying information on devices like seven-segment displays (2 Marks)

#### QUESTION FOUR (20 MARKS)

- a) i. Compare and contrast the functionalities of SR and JK flip-flops, including their truth tables and triggering conditions (4 Marks)
- ii. Design a circuit using an SR flip-flop and additional logic gates (e.g., AND, OR, NOT) to create a T-flip-flop (2 Marks). Draw the circuit diagram and explain its operation.
- iii. Briefly explain the concept of race-around condition in JK flip-flops and suggest a method to prevent it (2 Marks)
- b) i. Define a shift register and explain its basic operation, including the difference between left shift and right-shift registers (2 Marks)
- ii. Describe a situation where a 4-bit left-shift register would be useful in a digital circuit (2 Marks). Draw a simple example of its operation with an initial data value.
- iii. Briefly explain the difference between serial-in/parallel-out (SIPO) and parallel-in/parallel-out (PIPO) shift registers (2 Marks)
- c) i. Define a counter and explain its basic operation, including the concept of modulus in counters (2 Marks)

- d) ii. Design a 3-bit synchronous counter using JK flip-flops that counts from 0 to 7 and then repeats (modulus 8) (2 Marks). Draw the circuit diagram and explain its operation.
- e) iii. Briefly describe the difference between synchronous and asynchronous counters and give an example of each (2 Marks)

